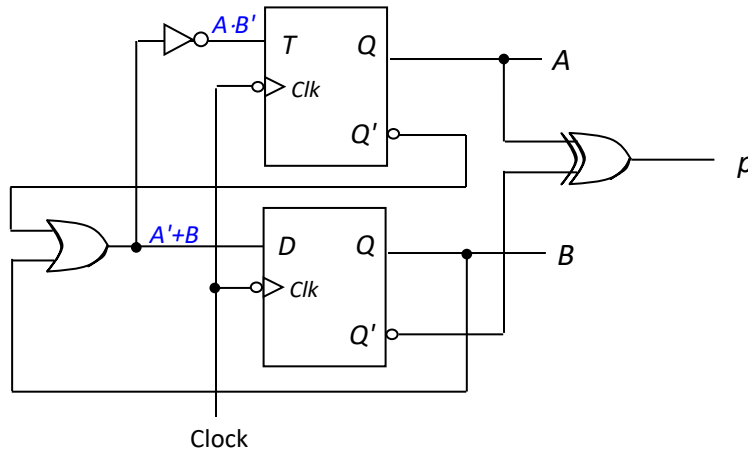


CS2100 Computer Organisation
Tutorial #9: Sequential Circuits
Answers to Selected Questions

Tutorial Questions

1. A four-state sequential circuit below consists of a **T flip-flop** and a **D flip-flop**. Analyze the circuit.



- (a) Complete the state table and hence draw the state diagram.
 (b) Assuming that the circuit is initially at state 0, what is the final state and the outputs generated after 3 clock cycles?

A state is called a **sink** if once the circuit enters this state, it never moves out of that state.


- (c) How many sinks are there for this circuit?
 (d) Which is likely to be an unused state in this circuit?

Answers:

(a)

$$\begin{aligned} p &= A \cdot B + A' \cdot B' \\ TA &= A \cdot B' \\ DB &= A' + B \end{aligned}$$


Present state		Output	Flip-flop inputs		Next state	
A	B	p	TA	DB	A+	B+
0	0	1	0	1	0	1
0	1	0	0	1	0	1
1	0	0	1	0	0	0
1	1	1	0	1	1	1

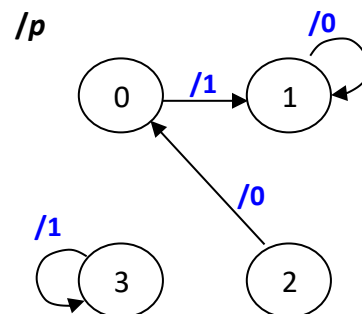

- (b) After 3 clock cycles, the circuit is in state 1, and it generated 100 as output.
 (c) There are 2 sinks: states 1 and 3.
 (d) State 3 is likely to be an unused state.

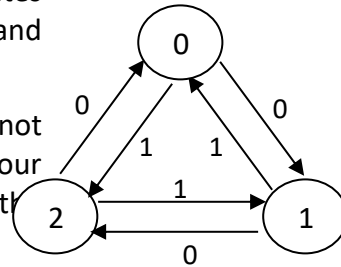
2. Given the state transition diagram on the right with states AB and input x , implement the circuit using ***JK flip-flops*** and the fewest number of logic gates.

Fill in the state table below and draw the circuit. You do not need to follow the simplest SOP expression in your implementation as that might not give you a circuit with the fewest logic gates.



Present state		Input x	Next state		Flip-flop A		Flip-flop B	
A	B		A^+	B^+	JA	KA	JB	KB
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

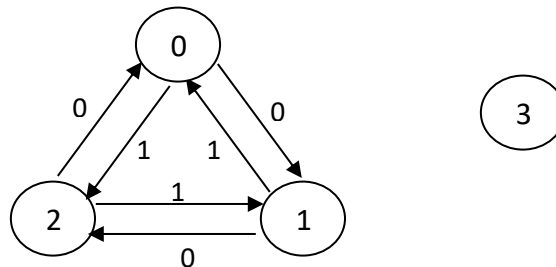State 3 is unused. Can you complete the following state diagram with the unused state?



A circuit is **self-correcting** if for some reason the circuit enters into any unused (invalid) state, it is able to transit to a valid state after a finite number of transitions. Is your circuit self-correcting, and why?

Answers:

Using K-maps to find simplified expressions for flip-flop inputs.

Present state		Input x	Next state		Flip-flop A		Flip-flop B	
A	B		A^+	B^+	JA	KA	JB	KB
0	0	0	0	1	0	d	1	d
0	0	1	1	0	1	d	0	d
0	1	0	1	0	1	d	d	1
0	1	1	0	0	0	d	d	1
1	0	0	0	0	d	1	0	d
1	0	1	0	1	d	1	1	d
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d

d = don't care

JA

	B			
	0	1	0	1
A	d	d	d	d
	x			

KA

	B			
	d	d	d	d
A	1	1	d	d
	x			

KB


	B			
	d	d	1	1
A	d	d	d	d
	x			

$$JA = B \cdot x' + B' \cdot x = B \oplus x$$

$$KA = 1$$


$$JB = A' \cdot x' + A \cdot x = A \odot x$$

$$KB = 1$$

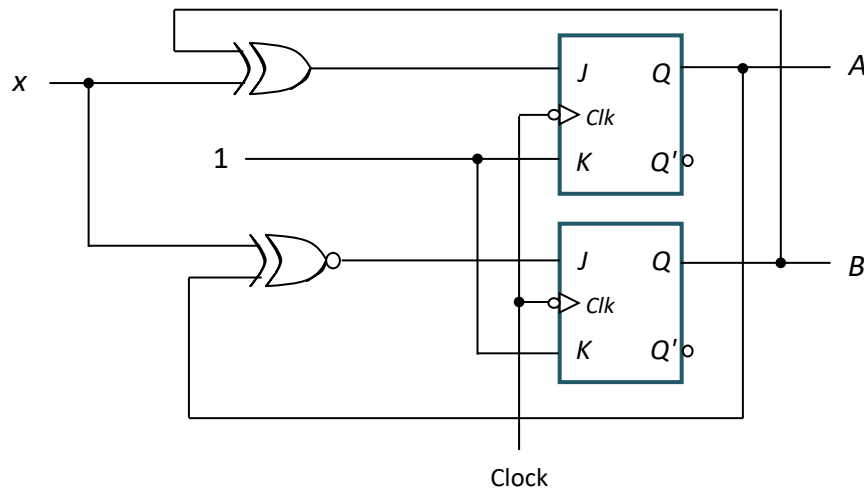

After committing the expressions for the flip-flop inputs, the don't-care values below are replaced with actual values (in parentheses). The state diagram with the unused state 3 is shown below. It is a self-correcting circuit, since there is an arrow out from state 3 to a used state.

Present state		Input x	Next state		Flip-flop A		Flip-flop B	
A	B		A^+	B^+	JA	KA	JB	KB
0	0	0	0	1	0	d(1)	1	d(1)
0	0	1	1	0	1	d(1)	0	d(1)
0	1	0	1	0	1	d(1)	d(1)	1
0	1	1	0	0	0	d(1)	d(0)	1
1	0	0	0	0	d(0)	1	0	d(1)
1	0	1	0	1	d(1)	1	1	d(1)
1	1	0	d(0)	d(0)	d(1)	d(1)	d(0)	d(1)
1	1	1	d(0)	d(0)	d(0)	d(1)	d(1)	d(1)

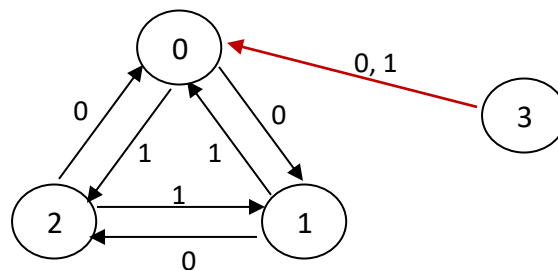


4. Pokemone Theme Park offers locker rental to its visitors. Visitors may purchase two types of token: Pokemoney \$1 (P\$1) and Pokemoney \$2 (P\$2). A locker's rental costs P\$3. When a visitor deposits P\$3 into the locker's token slot, its door will open.

Design a sequential circuit with states AB for the locker's door using D flip-flops. The circuit consists of 4 states representing the amount a visitor has deposited: 0, 1, 2 and 3 (or, in binary, $AB = 00, 01, 10$ and 11). The visitor can deposit only one token at a time. When the circuit reaches the final state 3, it remains in state 3 even if the visitor continues to put tokens into the slot. When the circuit is in state 2 and the visitor deposits a P\$2 token, the circuit goes into state 3.

The partial state diagram is shown below. The inputs x and y represent the P\$1 and P\$2 tokens respectively. The label on each arrow represents xy .

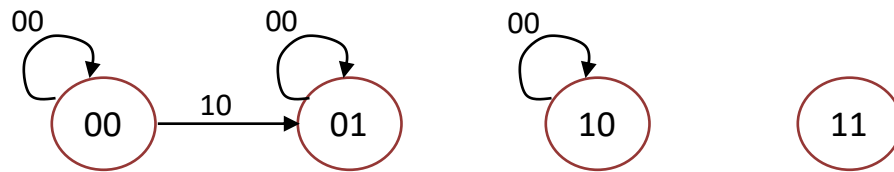
- (a) Draw and write the missing arrows and labels.



- (b) Write the **simplified SOP expressions** for the flip-flop inputs DA and DB .

Answers:

- (a)

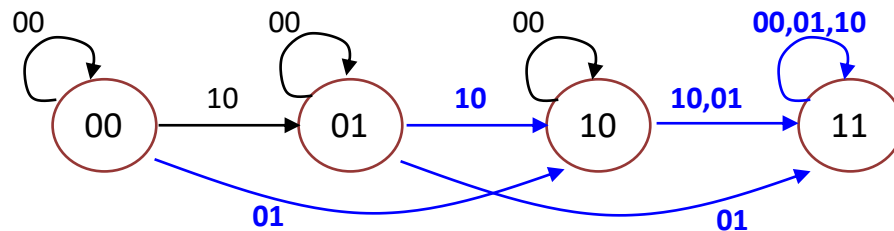

- (b)

$$DA = A + y + B \cdot x$$

$$DB = B \cdot x' + B' \cdot x + A \cdot y + A \cdot x \text{ or } DB = B \cdot x' + B' \cdot x + A \cdot y + A \cdot B$$