

CS2100

COMPUTER ORGANISATION

<http://www.comp.nus.edu.sg/~cs2100/>

## Lecture #20

---

# Pipelining

## Part I: Introduction



**NUS**  
National University  
of Singapore

School of  
Computing

# Lecture #20: Pipelining I

1. Introduction
2. MIPS Pipeline Stages
3. Pipeline Datapath
4. Pipeline Control
5. Pipeline Performance

# 1. Introduction: Inspiration




Assembly Line

**Simpler station tasks → more cars per hour.  
Simple tasks take less time, clock is faster.**



   
# 1. Introduction: Laundry

- **Ann, Brian, Cathy, Dave** each have one load of clothes to wash, dry, fold and stash
- **Washer** takes 30 minutes
- **Dryer** takes 30 minutes
- **“Folder”** takes 30 minutes
- **“Stasher”** takes 30 minutes to put clothes into drawers




# 1. Introduction: Sequential Laundry

 


- Sequential laundry takes 8 hours for 4 loads
- Steady state: 1 load every 2 hours
- If they learned **pipelining**, how long would laundry take?

# 1. Introduction: Pipelined Laundry

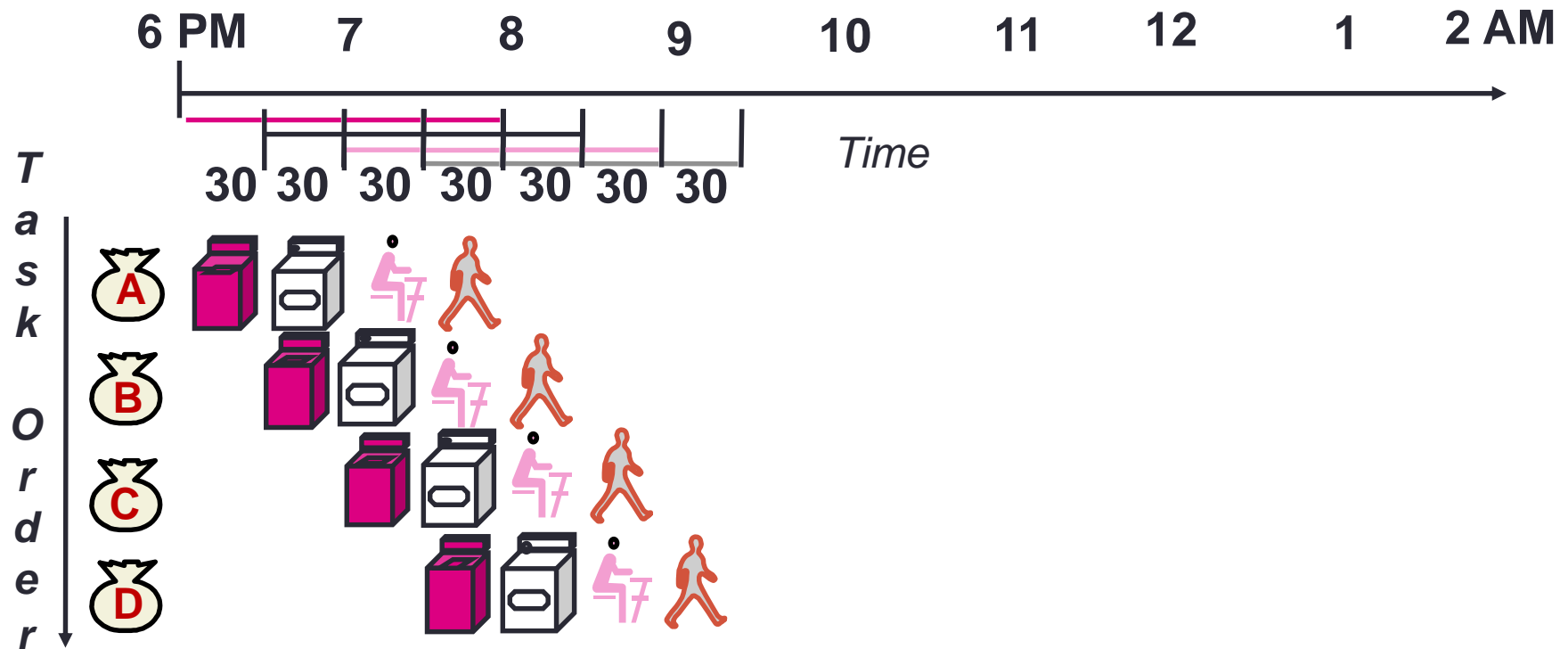


- Pipelined laundry takes 3.5 hours for 4 loads!
- Steady state: 1 load every 30 minutes
- Potential speedup =  $2 \text{ hr} / 30 \text{ min} = 4$  (no. of stages)
- Time to fill pipeline takes 2 hours  $\rightarrow$  speedup  $\downarrow$

# 1. Introduction: What If: Slow Dryer

 

- **Pipelined laundry now takes 5.5 hours!**
- Steady state: One load every 1 hour (dryer speed)
- **Pipeline rate is limited by the slowest stage**

# 1. Introduction: What If: Dependency

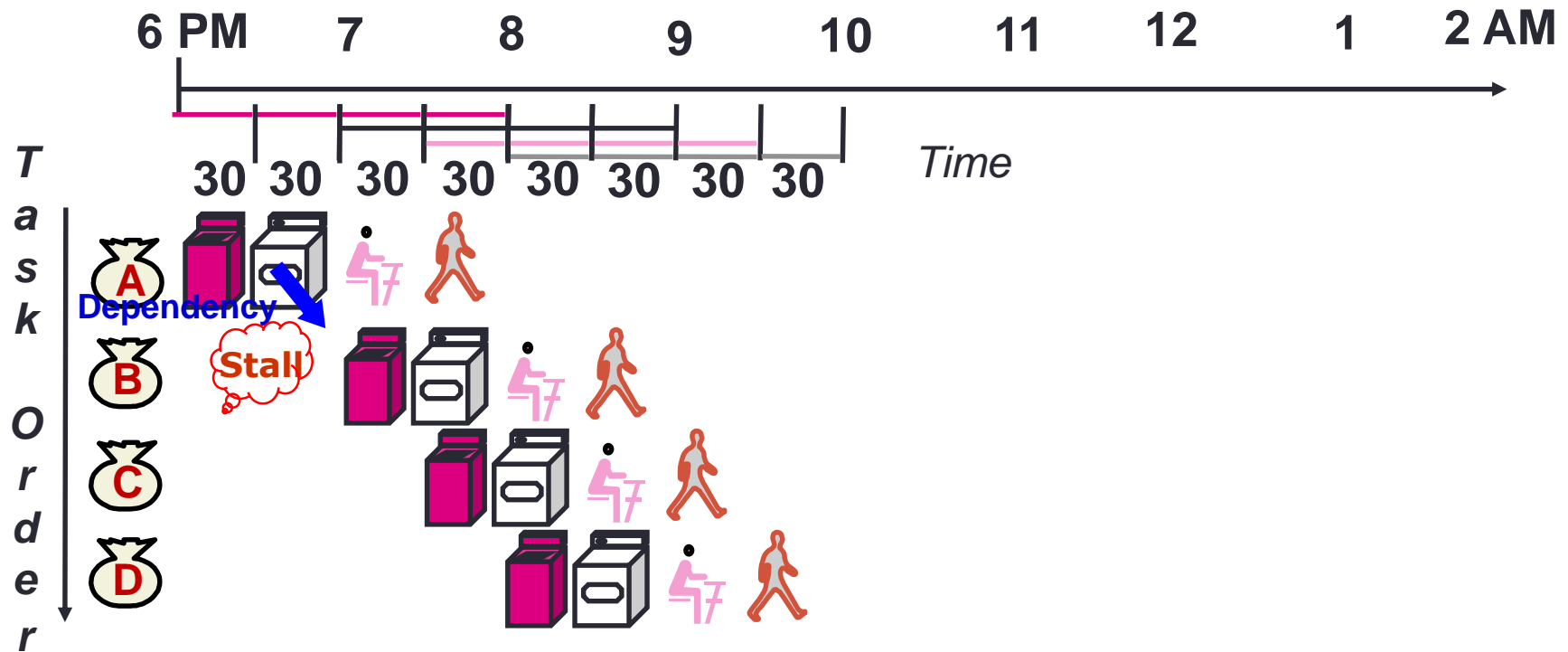

- Brian is using the laundry for the first time; he wants to see the outcome of one wash + dry cycle first before putting in his clothes
- **Pipelined laundry now takes 4 hours**




# 1. Introduction: Pipelining Lessons

- Pipelining doesn't help **latency** of single task:
  - It helps the **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Possible delays:
  - Pipeline rate limited by **slowest** pipeline stage
  - Stall for **dependencies**


## 2. MIPS Pipeline Stages (1/2)

- **Five** Execution Stages
  - **IF**: Instruction Fetch
  - **ID**: Instruction Decode and Register Read
  - **EX**: Execute an operation or calculate an address
  - **MEM**: Access an operand in data memory
  - **WB**: Write back the result into a register
- **Idea:**
  - **Each execution stage takes 1 clock cycle**
  - General flow of data is from one stage to the next
- **Exceptions:**
  - Update of PC and write back of register file – more about this later...

## 2. MIPS Pipeline Stages (2/2)

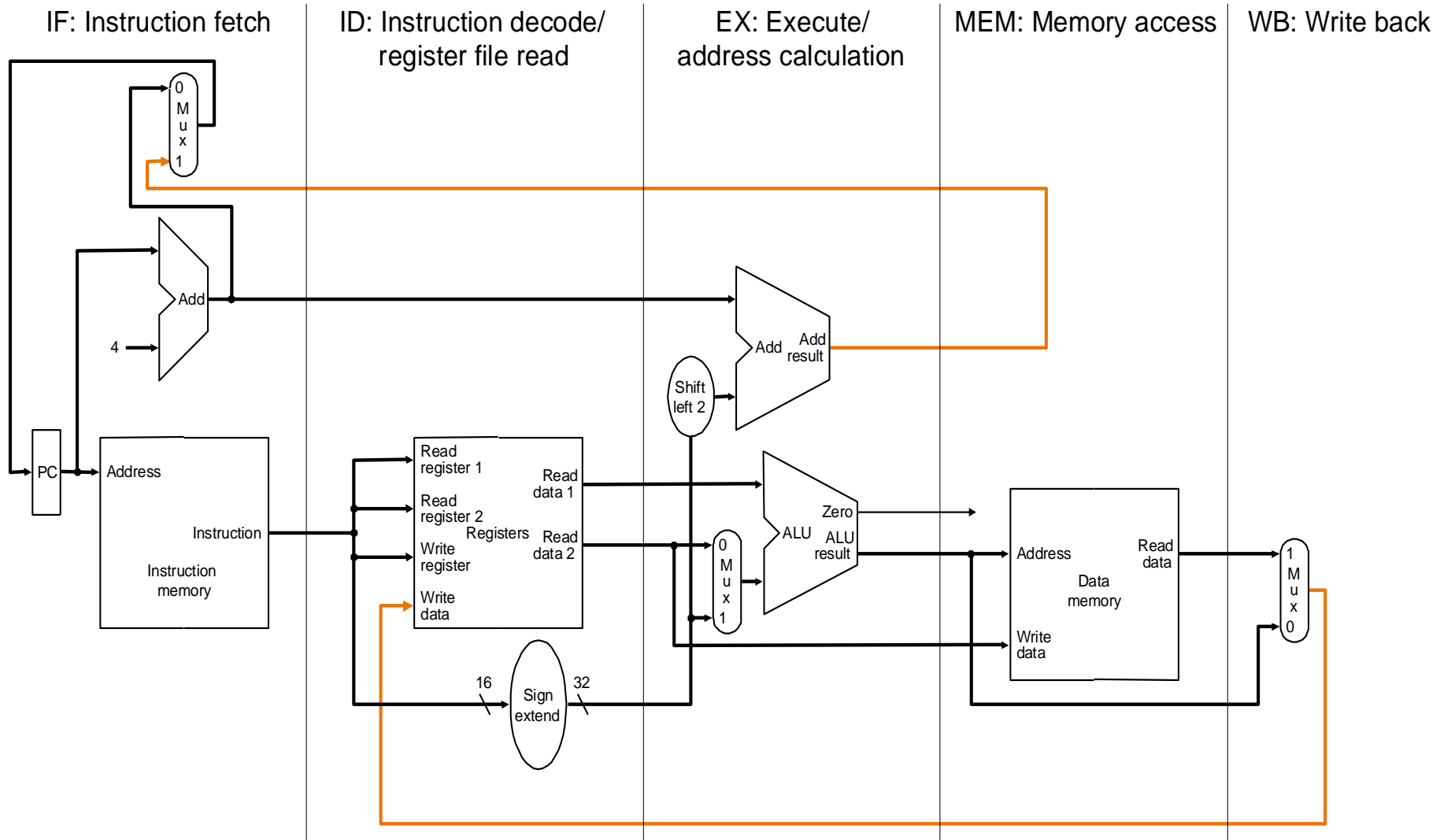

## 2. Pipelined Execution: Illustration

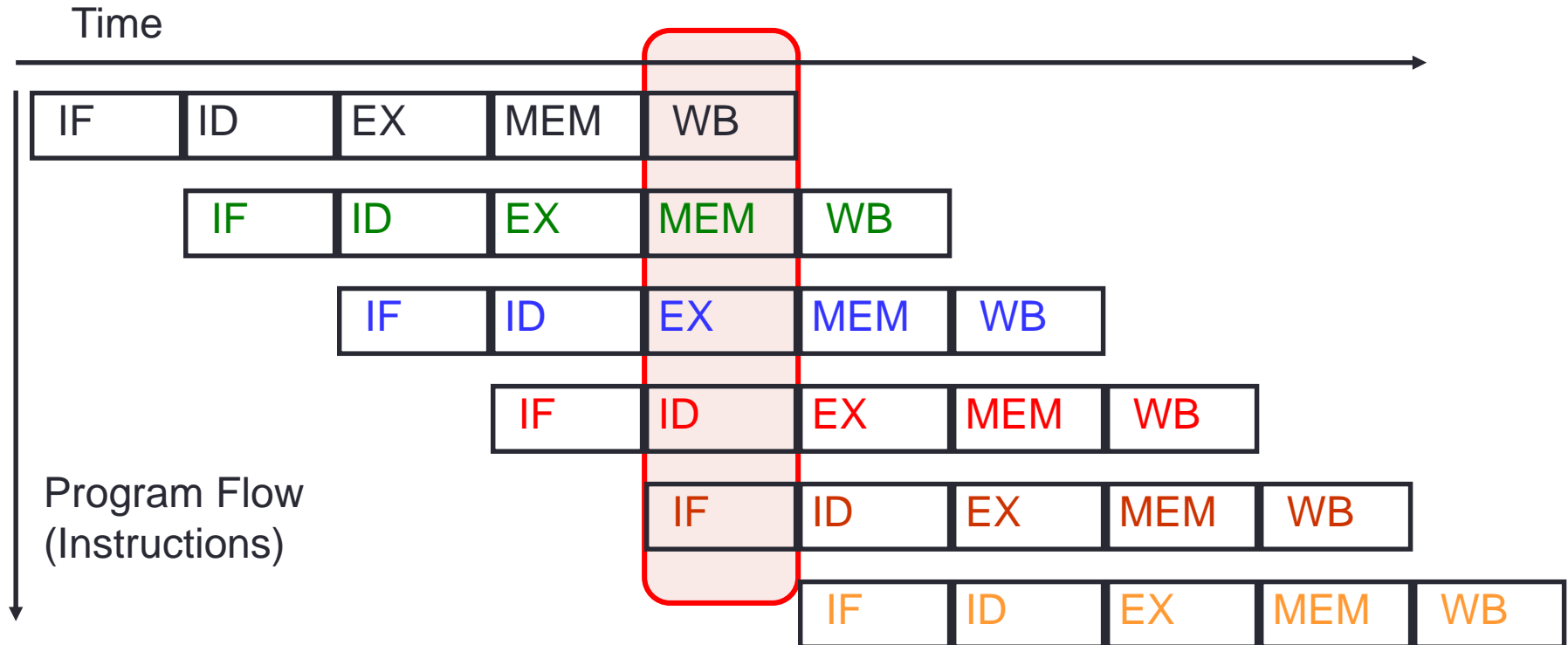

Several instructions  
are in the pipeline  
simultaneously!

### 3. MIPS Pipeline: Datapath (1/3)


- **Single-cycle** implementation:
  - Update all state elements (PC, register file, data memory) at the end of a clock cycle
- **Pipelined** implementation:
  - One cycle per pipeline stage
  - Data required for each stage needs to be stored separately (why?)

### 3. MIPS Pipeline: Datapath (2/3)


- Data used by **subsequent instructions**:
  - Store in programmer-visible state elements: **PC**, register file and memory
- Data used by **same instruction** in later pipeline stages:
  - Additional registers in datapath called **pipeline registers**
  - **IF/ID**: register between **IF** and **ID**
  - **ID/EX**: register between **ID** and **EX**
  - **EX/MEM**: register between **EX** and **MEM**
  - **MEM/WB**: register between **MEM** and **WB**
- Why no register at the end of **WB** stage?
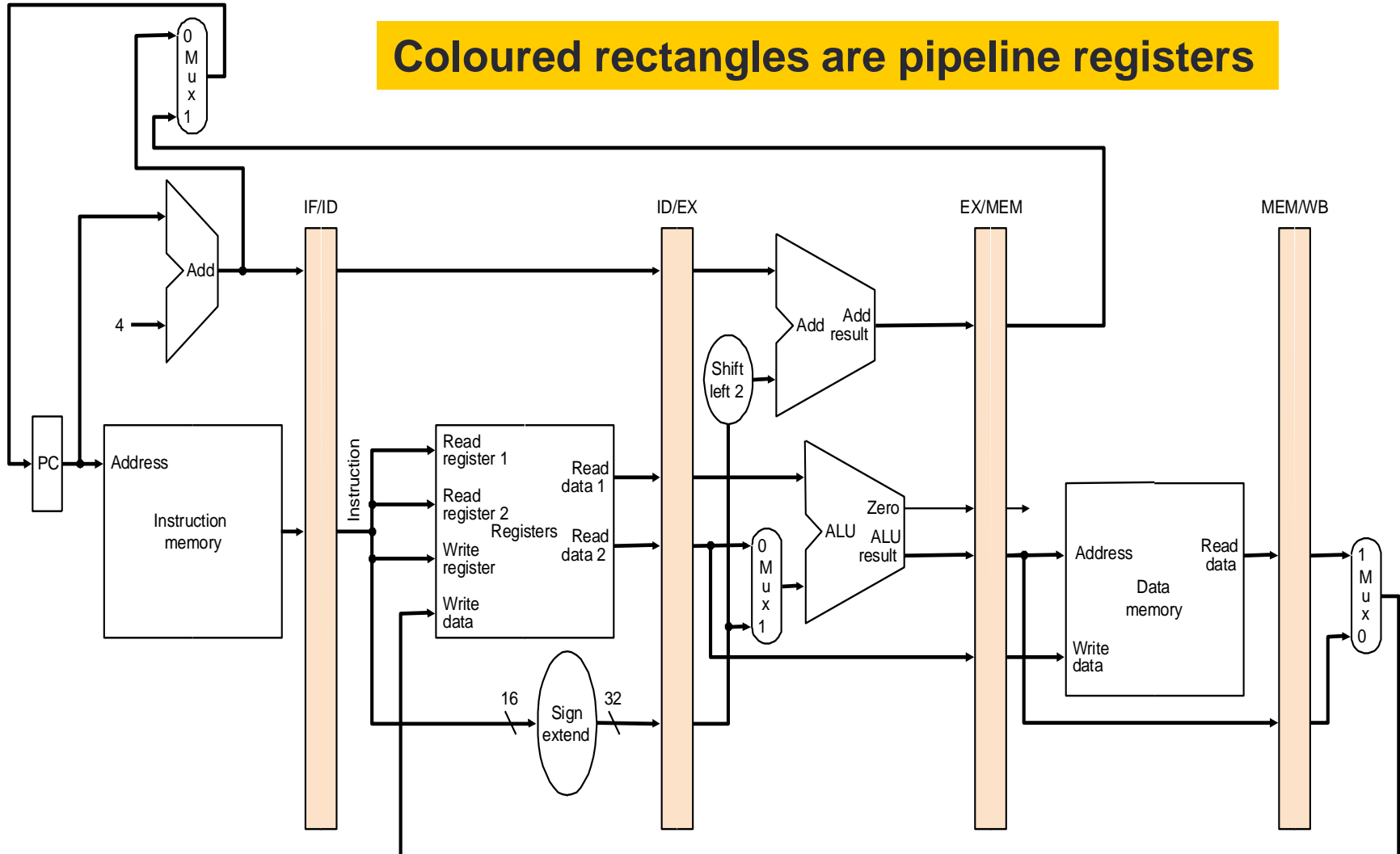
# 3. MIPS Pipeline: Datapath (3/3)

Coloured rectangles are pipeline registers




### 3. Pipeline Datapath: **IF** Stage

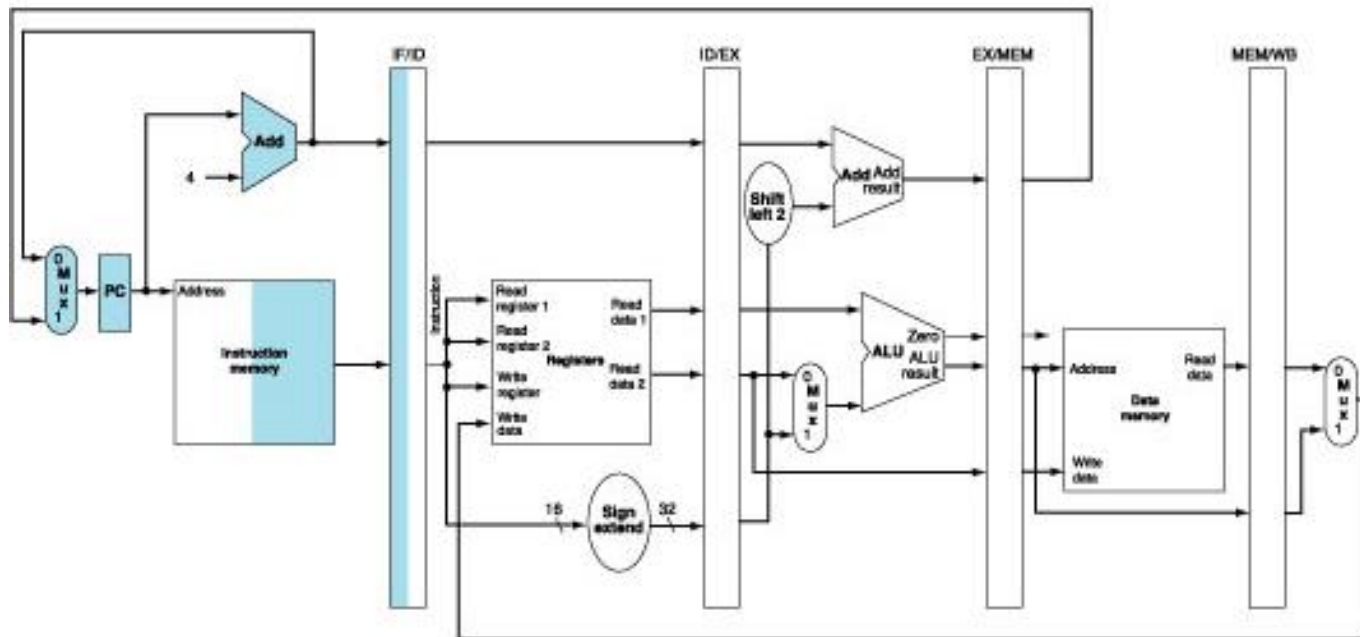

- At the end of a cycle, **IF/ID** receives (stores):
  - Instruction read from InstructionMemory[ PC ]
  - PC + 4
- PC + 4
  - Also connected to one of the MUX's inputs (another coming later)



### 3. Pipeline Datapath: ID Stage

 


**At the beginning of a cycle**  
**IF/ID** register supplies:

- ❖ Register numbers for reading two registers
- ❖ 16-bit offset to be sign-extended to 32-bit

**At the end of a cycle**  
**ID/EX** receives:

- ❖ Data values read from register file
- ❖ 32-bit immediate value
- ❖  $PC + 4$

### 3. Pipeline Datapath: **EX** Stage

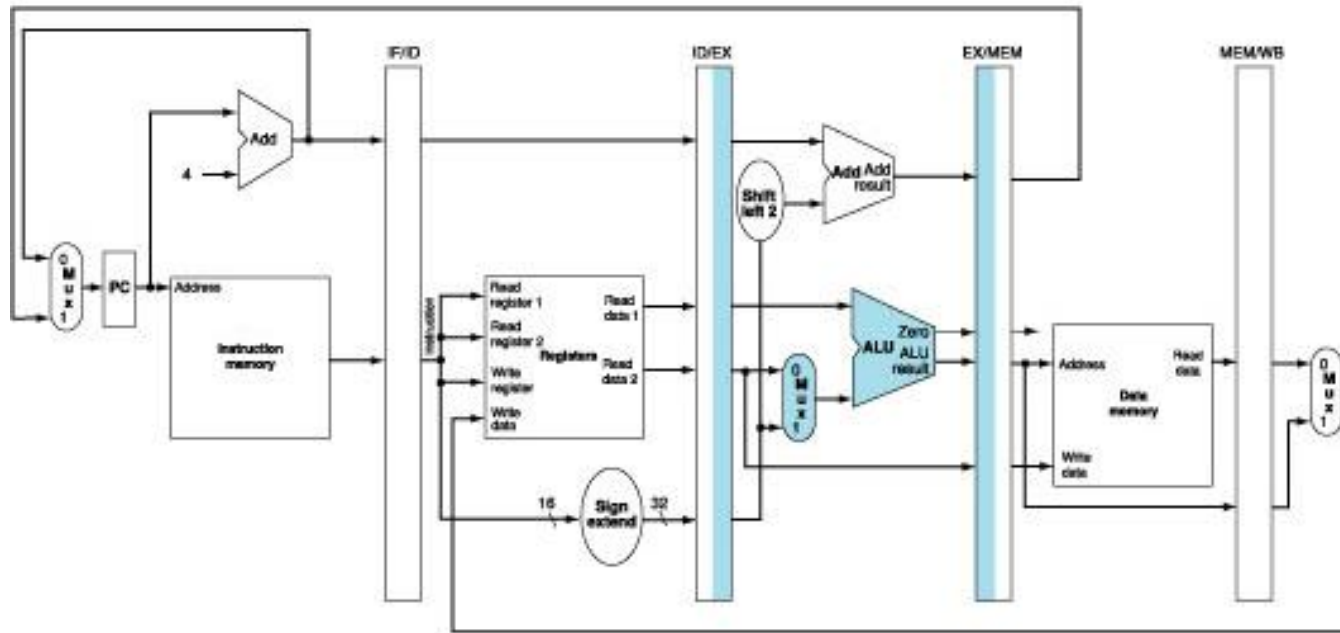


**At the beginning of a cycle**  
**ID/EX** register supplies:

- ❖ Data values read from register file
- ❖ 32-bit immediate value
- ❖  $PC + 4$

**At the end of a cycle**  
**EX/MEM** receives:

- ❖  $(PC + 4) + (\text{Immediate} \times 4)$
- ❖ ALU result
- ❖ **isZero?** signal
- ❖ Data Read 2 from register file

### 3. Pipeline Datapath: **MEM** Stage

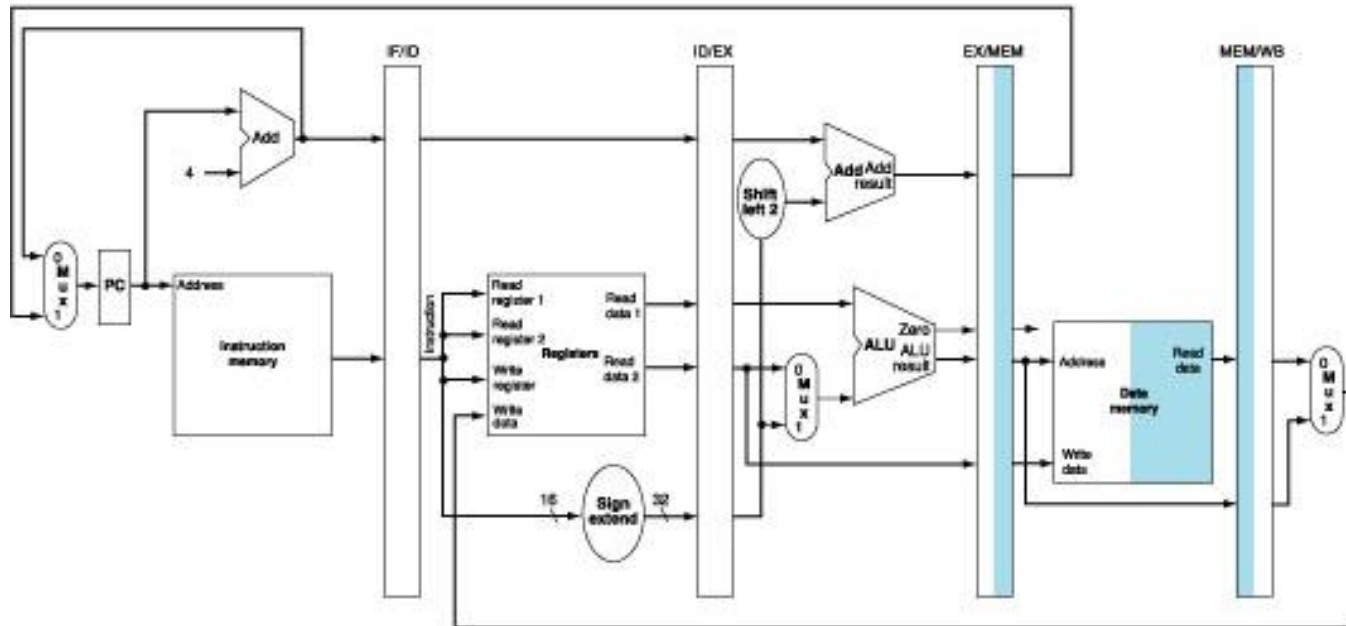


**At the beginning of a cycle**  
**EX/MEM** register supplies:

- ❖  $(PC + 4) + (Immediate \times 4)$
- ❖ ALU result
- ❖ `isZero?` signal
- ❖ Data Read 2 from register file

**At the end of a cycle**  
**MEM/WB** receives:

- ❖ ALU result
- ❖ Memory read data

### 3. Pipeline Datapath: **WB Stage**

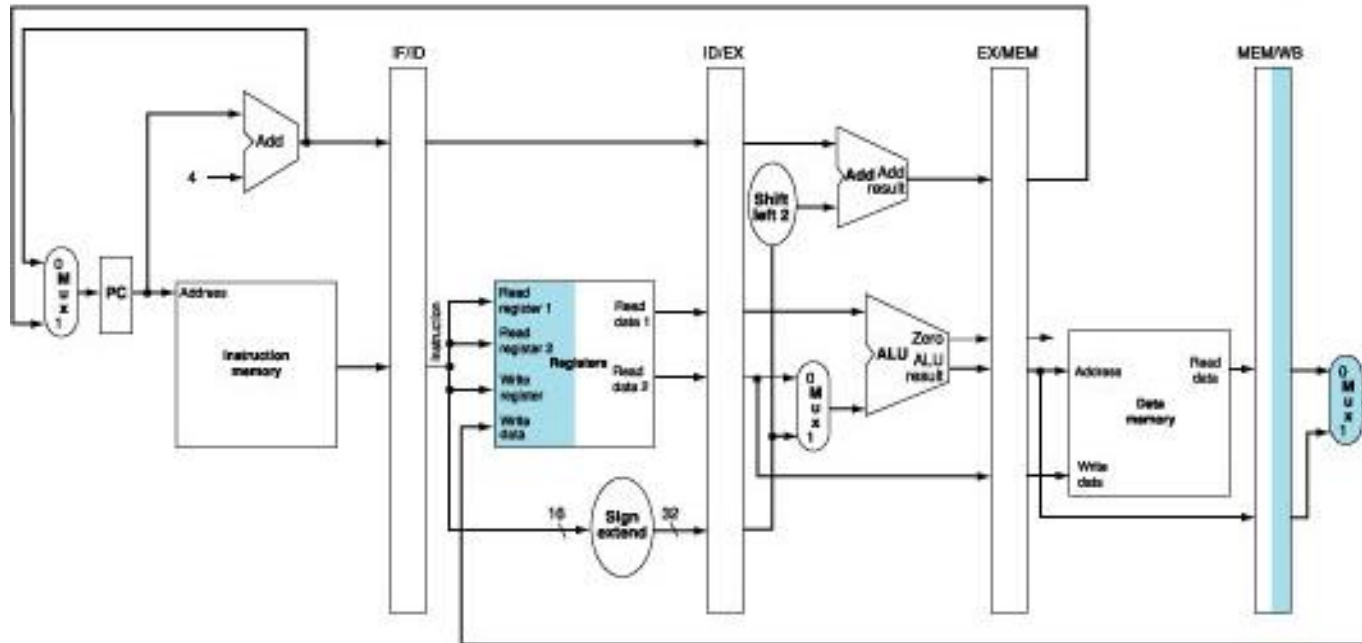

At the beginning of a cycle  
**MEM/WB** register supplies:

- ❖ ALU result
- ❖ Memory read data


At the end of a cycle

- ❖ Result is written back to register file (if applicable)
- ❖ **There is a bug here.....**

### 3. Corrected Datapath (1/2)


- Observe the “Write register” number
  - Supplied by the **IF/ID** pipeline register
  - ➔ It is NOT the correct write register for the instruction now in **WB** stage!
- **Solution:**
  - Pass “Write register” number from **ID/EX** through **EX/MEM** to **MEM/WB** pipeline register for use in **WB** stage
  - i.e. let the "Write register" number follows the instruction through the pipeline until it is needed in WB stage

# 3. Corrected Datapath (2/2)

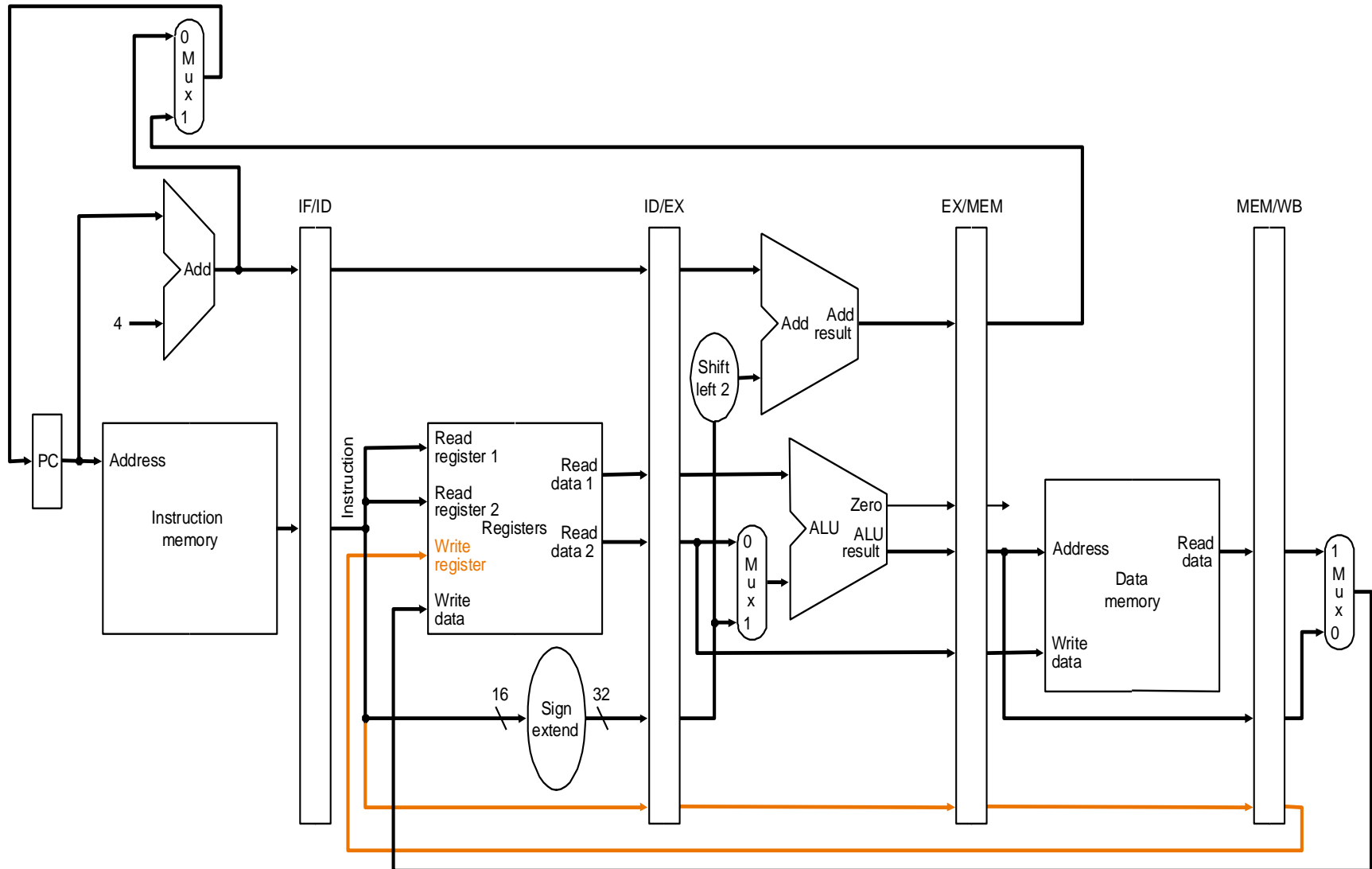

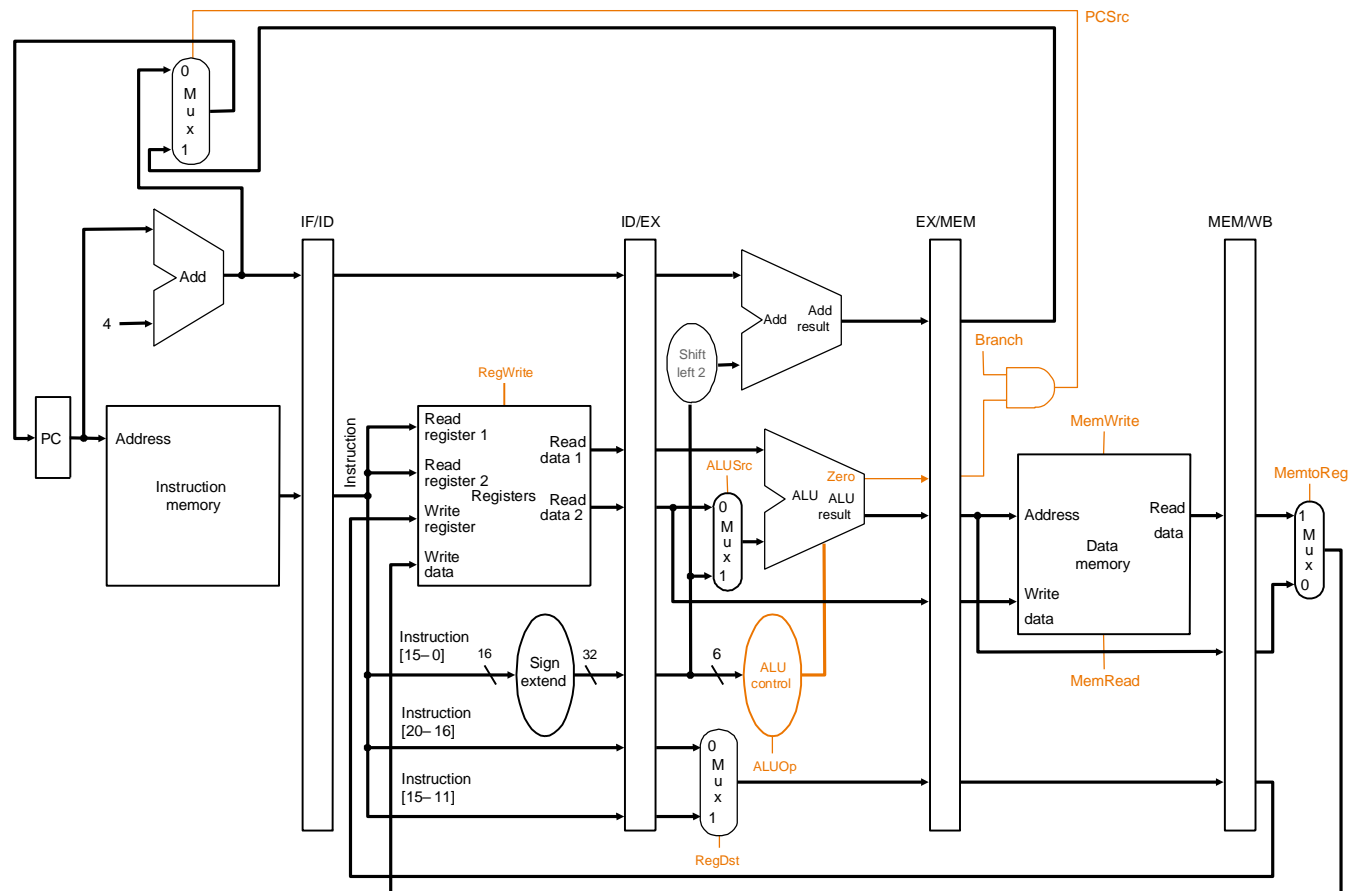
## 4. Pipeline Control: Main Idea

- Same control signals as single-cycle datapath
- Difference:** Each control signal belongs to a particular pipeline stage



# 4. Pipeline Control: Try it!

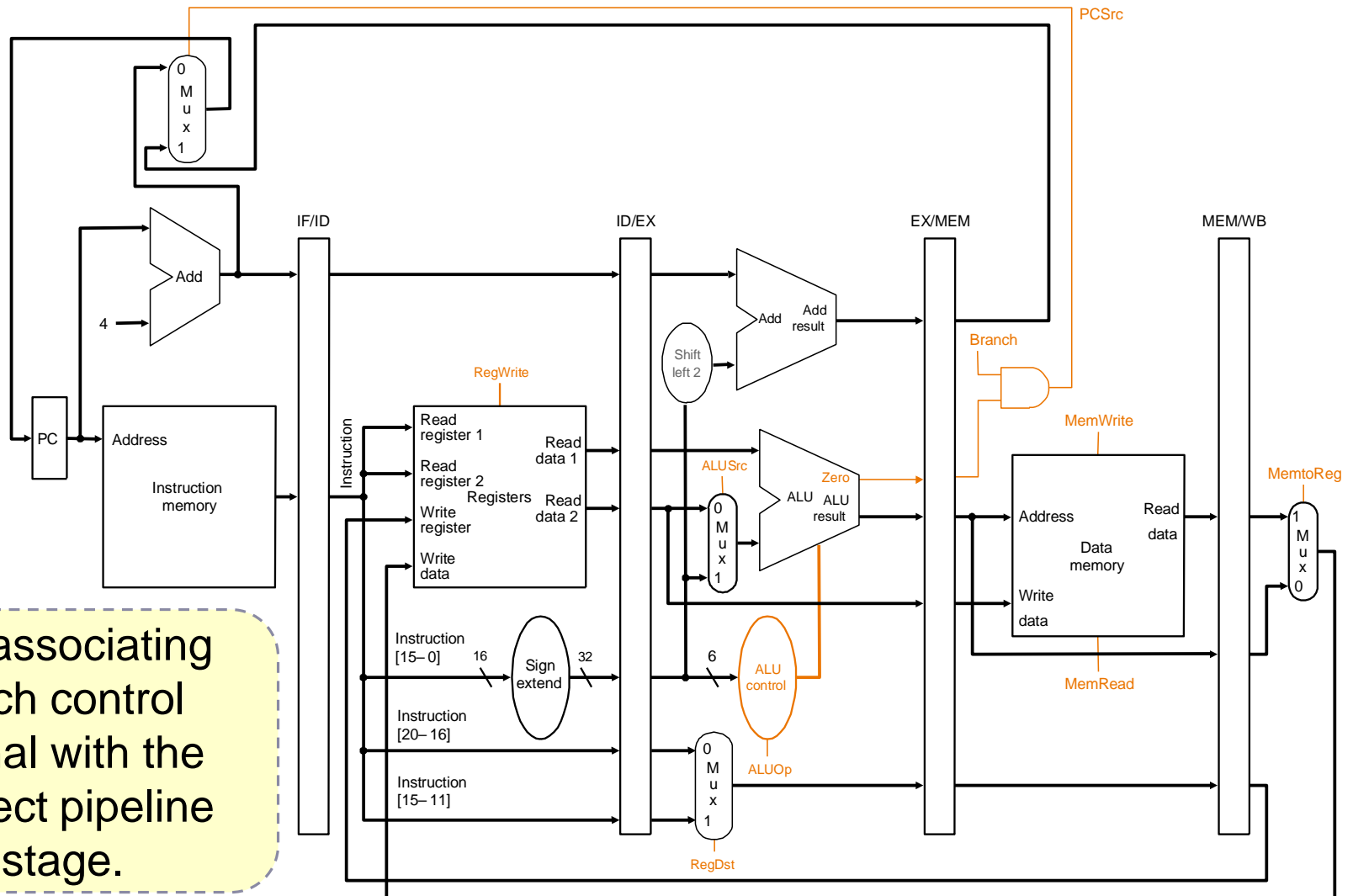




## 4. Pipeline Control: Grouping

- Group control signals according to pipeline stage


	RegDst	ALUSrc	MemTo Reg	Reg Write	Mem Read	Mem Write	Branch	ALUop	
								op1	op0
R-type	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

	EX Stage				MEM Stage			WB Stage	
	RegDst	ALUSrc	ALUop		Mem Read	Mem Write	Branch	MemTo Reg	Reg Write
			op1	op0					
R-type	1	0	1	0	0	0	0	0	1
lw	0	1	0	0	1	0	0	1	1
sw	X	1	0	0	0	1	0	X	0
beq	X	0	0	1	0	0	1	X	0

## 4. Pipeline Control: Implementation

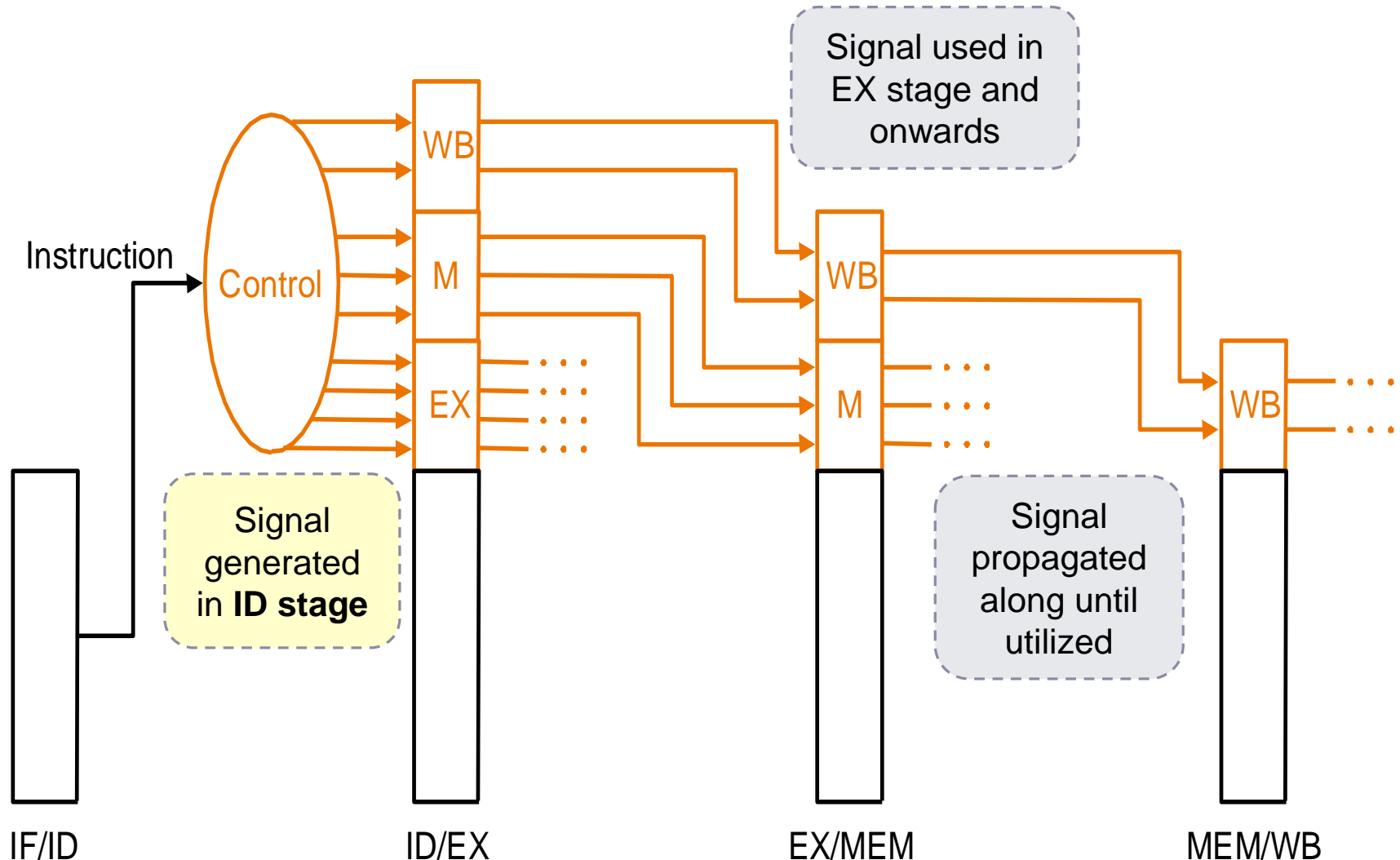

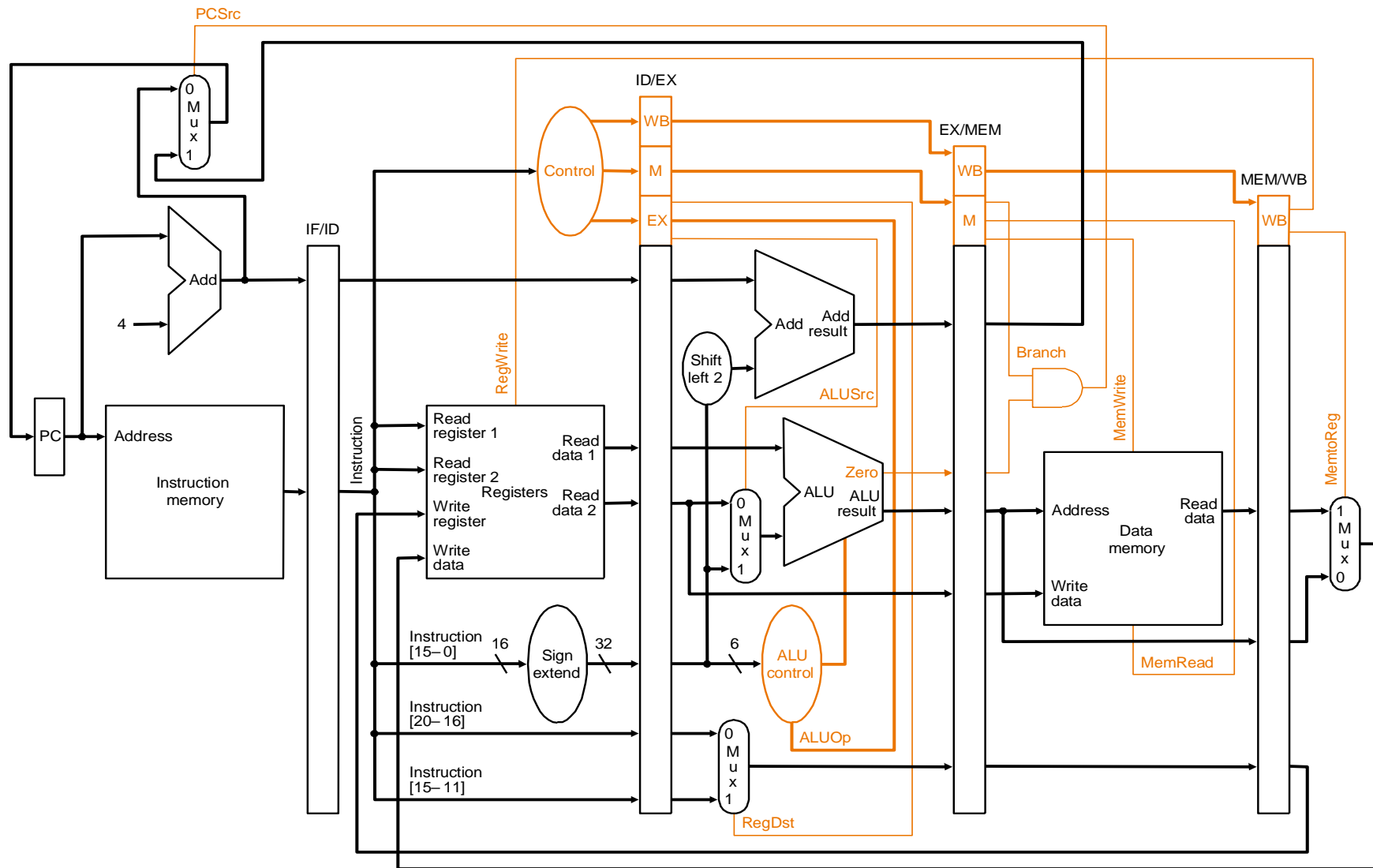
# 4. Pipeline Control: Datapath and Control




## 5. Different Implementations


### Single-Cycle

 

### Multi-Cycle

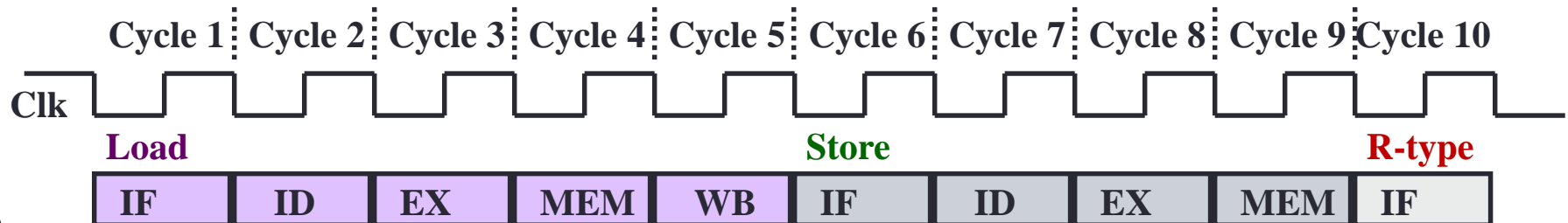

### Pipeline

 

## 5. Single Cycle Processor: Performance

- Cycle time:
  - $CT_{seq} = \sum_{k=1}^N T_k$
  - $T_k$  = Time for operation in stage k
  - N = Number of stages
- Total Execution Time for **I** instructions:
  - $Time_{seq} = Cycles \times CycleTime$   
 $= I \times CT_{seq} = I \times \sum_{k=1}^N T_k$

## 5. Single Cycle Processor: Example

Instruction	Inst Mem	Reg read	ALU	Data Mem	Reg write	Total
ALU	2	1	2		1	6
lw	2	1	2	2	1	8
sw	2	1	2	2		7
beq	2	1	2			5

- **Cycle Time**
  - Choose the longest total time = **8ns**
- To execute **100 instructions**:
  - **$100 \times 8\text{ns} = 800\text{ns}$**

## 5. Multi-Cycle Processor: Performance

- Cycle time:
  - $CT_{multi} = \max(T_k)$
  - $\max(T_k)$  = longest stage duration among the N stages
- Total Execution Time for **I** instructions:
  - $Time_{multi} = Cycles \times CycleTime$   
 $= I \times \textit{Average CPI} \times CT_{multi}$
  - Average CPI is needed because each instruction takes different number of cycles to finish

## 5. Multi-Cycle Processor: Example

Instruction	Inst Mem	Reg read	ALU	Data Mem	Reg write	Total
ALU	2	1	2		1	6
lw	2	1	2	2	1	8
sw	2	1	2	2		7
beq	2	1	2			5

- **Cycle Time**
  - Choose the longest stage time = **2ns**
- To execute **100 instructions**, with a given **average CPI of 4.6**
  - $100 \times 4.6 \times 2\text{ns} = 920\text{ns}$



## 5. Pipeline Processor: Performance

- Cycle Time:
  - $CT_{pipeline} = \max(T_k) + T_d$
  - $\max(T_k)$  = longest time among the N stages
  - $T_d$  = Overhead for pipelining, e.g. pipeline register
- Cycles needed for **I** instructions:
  - $I + N - 1$
  - $N - 1$  is the cycles wasted in filling up the pipeline
- Total Time needed for **I** instructions :
  - $Time_{pipeline} = Cycle \times CT_{pipeline}$   
 $= (I + N - 1) \times (\max(T_k) + T_d)$

## 5. Pipeline Processor: Example

Instruction	Inst Mem	Reg read	ALU	Data Mem	Reg write	Total
ALU	2	1	2		1	6
lw	2	1	2	2	1	8
sw	2	1	2	2		7
beq	2	1	2			5

- **Cycle Time**
  - assume pipeline register delay of **0.5ns**
  - longest stage time + overhead = **2 + 0.5 = 2.5ns**
- To execute **100 instructions**:
  - **$(100 + 5 - 1) \times 2.5\text{ns} = 260\text{ns}$**

## 5. Pipeline Processor: Ideal Speedup (1/2)

- Assumptions for ideal case:
  - Every stage takes the same amount of time:  
$$\rightarrow \sum_{k=1}^N T_k = N \times T_k$$
  - No pipeline overhead  $\rightarrow T_d = 0$
  - Number of instructions **I**, is much larger than number of stages, **N**
- Note: The above also shows **how pipeline processor loses performance**

## 5. Pipeline Processor: Ideal Speedup (2/2)

$$\blacksquare \text{Speedup}_{\text{pipeline}} = \frac{\text{Time}_{\text{seq}}}{\text{Time}_{\text{pipeline}}}$$

$$= \frac{I \times \sum_{k=1}^N T_k}{(I+N-1) \times (\max(T_k) + T_d)}$$

$$= \frac{I \times N \times T_k}{(I+N-1) \times T_k}$$

$$\approx \frac{I \times N \times T_k}{I \times T_k}$$

$$\approx N$$

### Conclusion:

Pipeline processor can gain **N** times speedup, where **N** is the number of pipeline stages

# Review Question

- Given this code:

```
add $t0, $s0, $s1  
sub $t1, $s0, $s1  
sll $t2, $s0, 2  
srl $t3, $s1, 2
```

- a) How many cycles will it take to execute the code on a single-cycle datapath?
- b) How long will it take to execute the code on a single-cycle datapath, assuming a 100 MHz clock?
- c) How many cycles will it take to execute the code on a 5-stage MIPS pipeline?
- d) How long will it take to execute the code on a 5-stage MIPS pipeline, assuming a 500 MHz clock?

# End of File