

**CS2100 Computer Organisation**  
**AY2021/22 Semester 1**  
**Assignment 2 Answer Sheet**

<b>FULL NAME:</b>	
<b>STUDENT ID:</b> E.g., <AxxxxxxxY>	
<b>TUTORIAL GROUP:</b>	

**Question 0. Submission instructions (3 marks)**

a. Name your file with your student number (eg: AxxxxxxxY>.pdf). (1 mark)	<b>Y / N</b>
b. Submit your assignment as a single PDF file. (1 mark)	<b>Y / N</b>
c. Your submission has your tutorial group number, student number and name. (1 mark)	<b>Y / N</b>

**Question 1. Datapath (8 marks)**


Field	Value
RegDst	
MemRead	
MemWrite	
ALUSrc	
RegWrite	
Instruction[31-26] *	0b
Instruction[25-21] *	0b
Instruction[20-16] *	0b
Instruction[15-11] *	0b
Instruction[5-0] *	0b
❶ * (output from sign-extend)	0x
❷ *	0x
❸ *	0x
❹ * (read data 2)	0x
❺ *	0x
❻ (ALU control output)	

**Question 2. Simplification (14 marks)**

(a)  $B \cdot Y \cdot E' \cdot (A' \cdot X + A \cdot X' + A \cdot X + A' \cdot X') + B' \cdot L \cdot U \cdot E' \cdot S' \cdot K \cdot Y + Y \cdot E' \cdot S'$

[6 marks]


(b)

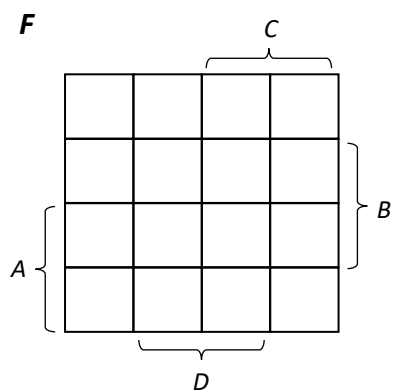

[4 marks]

#PIs	
#EPIs	
Simplest SOP	
Simplest POS	

(c)

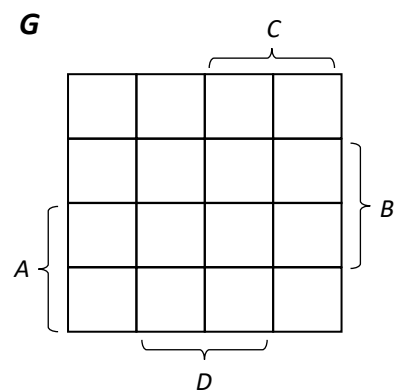


[4 marks]

#PIs	
#EPIs	
Simplest SOP	
Simplest POS	

**Question 3. Circuit Design (8 marks)**

(a) [2 marks]

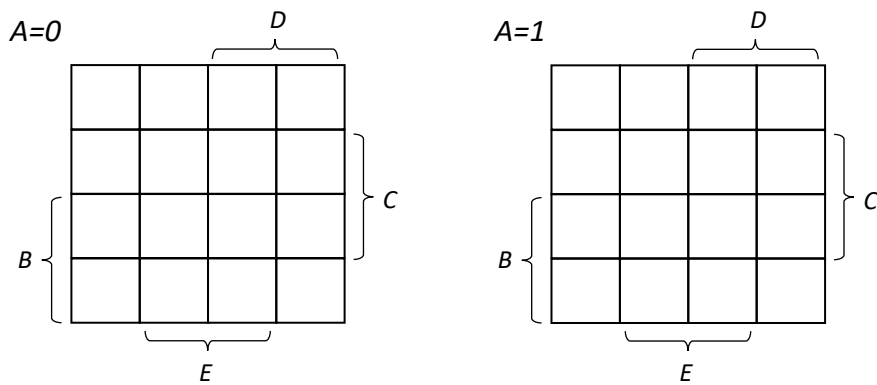

(b) Write out the simplified SOP expression for  $M$ .

[3 marks]


c) Draw the circuit for  $V$ .

[3 marks]

**Question 4. Block-level design (7 marks)**

(a)  $F(A,B,C,D) = \sum m(1, 4, 5, 6, 7, 13)$


[3 marks]

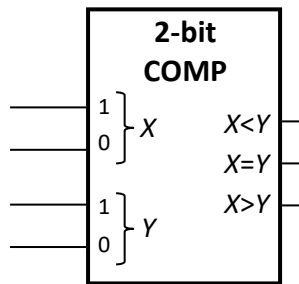

(b)  $G(A,B,E) = \sum m(3,5)$

$H(A,B,E) = \sum m(1,2,4,6)$

[4 marks]

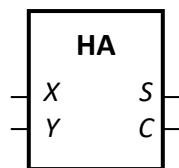

A	B	E					
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

(Add more columns to the table if there are insufficient columns.)