

CS2100 Computer Organisation
AY2021/22 Semester 1
Assignment 2 Answer Sheet

FULL NAME:	Toh Jia-Yih Ronald
STUDENT ID: E.g., <AxxxxxxxY>	A0199937B
TUTORIAL GROUP:	T02

Question 0. Submission instructions (3 marks)

a. Name your file with your student number (eg: AxxxxxxxY>.pdf). (1 mark)	Y
b. Submit your assignment as a single PDF file. (1 mark)	Y
c. Your submission has your tutorial group number, student number and name. (1 mark)	Y

Question 1. Datapath (8 marks)

Field	Value
RegDst	X
MemRead	0
MemWrite	1
ALUSrc	1
RegWrite	0
Instruction[31-26] *	0b 101011
Instruction[25-21] *	0b 11101
Instruction[20-16] *	0b 10010
Instruction[15-11] *	0b 11111
Instruction[5-0] *	0b 11000
❶ * (output from sign-extend)	0x FFFF FFD8
❷ *	0x 0000 0000
❸ *	0x 0000 00A4
❹ * (read data 2)	0x 0004 0200
❺ *	0x 7FFF F01E
❻ (ALU control output)	0010

Question 2. Simplification (14 marks)

(a) $B \cdot Y \cdot E' \cdot (A' \cdot X + A \cdot X' + A \cdot X + A' \cdot X') + B' \cdot L \cdot U \cdot E' \cdot S' \cdot K \cdot Y + Y \cdot E' \cdot S'$

[6 marks]

$B \cdot Y \cdot E' \cdot (1) + B' \cdot L \cdot U \cdot E' \cdot S' \cdot K \cdot Y + Y \cdot E' \cdot S'$	Complement Law
$B \cdot Y \cdot E' + B' \cdot L \cdot U \cdot E' \cdot S' \cdot K \cdot Y + Y \cdot E' \cdot S'$	One Element Law
$B \cdot Y \cdot E' + Y \cdot E' \cdot S' \cdot (B' \cdot L \cdot U \cdot K + 1)$	Distributive Law
$B \cdot Y \cdot E' + Y \cdot E' \cdot S'$	One Element Law
$Y \cdot E' \cdot (B + S')$	Distributive Law

(b)

F

		$\overbrace{\hspace{1.5cm}}^C$			
		0	X	1	0
		0	X	1	1
$\underbrace{\hspace{0.5cm}}^A$		0	X	0	1
		0	X	1	0
		$\underbrace{\hspace{1.5cm}}^D$			
				$\underbrace{\hspace{1.5cm}}^R$	

[4 marks]

#PIs	4
#EPIs	3
Simplest SOP	$B \cdot C \cdot D' + A' \cdot D + B' \cdot D$
Simplest POS	$C \cdot (B + D') \cdot (A' + B' + D')$

(c)

G

		$\overbrace{\hspace{1.5cm}}^C$			
		0	0	1	1
		X	0	0	1
$\underbrace{\hspace{0.5cm}}^A$	$\underbrace{\hspace{0.5cm}}$	X	0	X	1
		1	X	X	1
		$\underbrace{\hspace{1.5cm}}^D$			

$\underbrace{\hspace{1.5cm}}^R$

[4 marks]

#PIs	6
#EPIs	3
Simplest SOP	$A \cdot B' + B' \cdot C + C \cdot D'$
Simplest POS	$(A + C) \cdot (B' + D')$

Question 3. Circuit Design (8 marks)

(a) [2 marks]

$A=0$					
		D			
		X	X	X	X
		X	X	1	X
B		1	1	1	0
		0	1	1	0
		E			

$A=1$					
		D			
		0	1	1	0
		0	1	1	1
B		0	1	1	0
		0	1	1	0
		E			


(b) Write out the simplified SOP expression for M .

[3 marks]

$$E + A' \cdot C \cdot D' + A \cdot C \cdot D$$

c) Draw the circuit for V .

[3 marks]

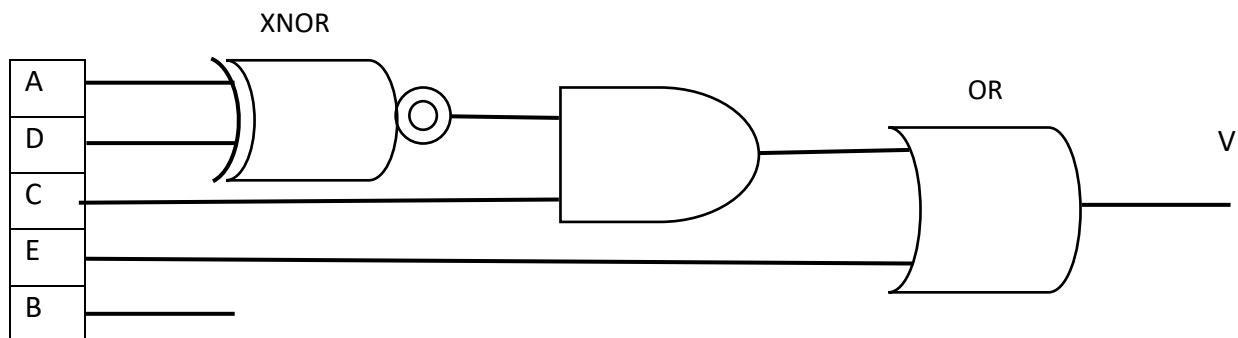


*Labelling xnor and or in case drawing is too bad ._.

Question 4. Block-level design (7 marks)

(a) $F(A,B,C,D) = \sum m(1, 4, 5, 6, 7, 13)$


[3 marks]

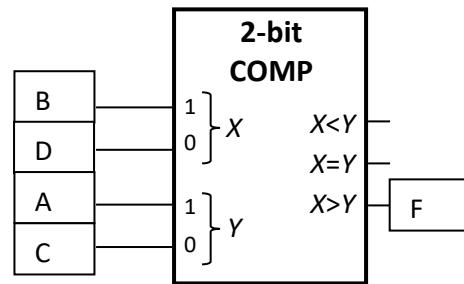

(b) $G(A,B,E) = \sum m(3,5)$

$H(A,B,E) = \sum m(1,2,4,6)$

[4 marks]

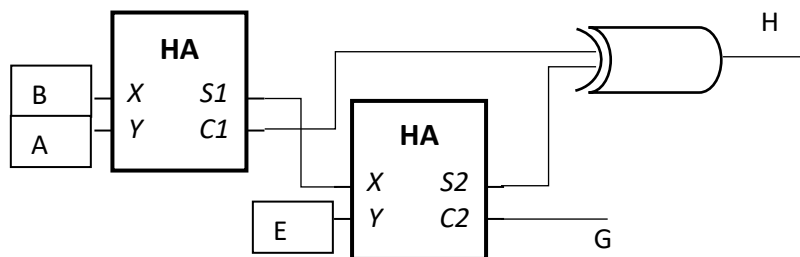

A	B	E	G	H	C1	S1	$C2 = S1 \cdot E = G$	$S2 = A \oplus B \oplus E$	$H = A \oplus B \oplus E \oplus C1$
0	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	1	1
0	1	0	0	1	0	1	0	1	1
0	1	1	1	0	0	1	1	0	0
1	0	0	0	1	0	1	0	1	1
1	0	1	1	0	0	1	1	0	0
1	1	0	0	1	1	0	0	0	1
1	1	1	0	0	1	0	0	1	0

(Add more columns to the table if there are insufficient columns.)